Intelligent Charger Service Manual

Li-ion battery charging chips mainly IC CHK0501 as the core components, plus a switch-mode stabilized voltage power and a number of external components.

1. Li-ion Battery Charging Chip CHK0501

CHK0501's internal circuit is composed of the reference voltage circuit, sampling circuit and short circuit protection circuit and so on. Chart 1 is its pin indication, where PIN 1 is the power negative input; PIN 2 is the LED driver output control; PIN 3 is the power positive input; PIN 4 is the charging tube control output; PIN 5 is the temperature compare input; PIN 6 is the undervoltage compare input; PIN 7 is the battery positive voltage input; PIN 8 is the current detection input and power negative. (See chart 1)

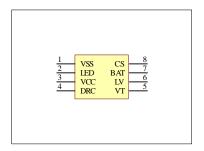


Chart 1 CHK0501's pin

2. Charger's Operation Principle

(1) Switch-mode stabilized voltage power

switch-mode stabilized voltage power is grid JP12 AC voltage directly rectified by D61, D62, D63, D64, filtered into a high-voltage DC, and transformed by the high-frequency transformer TR44 and power switching transistors U52 into low-voltage AC, and then rectified by the D44 low-voltage, filter output DC voltage. If remove diode D12, through the diode D11 and DC Block JK11 connect charger (adapter).

(2) Trickle, Constant Current, and Constant Voltage three charging mode

R34, R35, R36, R37, R15, R19, R39 are used to adjust the constant voltage and undervoltage determine voltage, Li-ion battery charging chips CHK0501 change the

charging method of charge tube T11 according to constant voltage and undervoltage determine voltage (trickle, constant current, constant voltage). Adjusting the value of R21, R22 can change the constant charging current.

(3) Temperature detect and current detect

Set the value of R20, Li-ion battery charging chip CHK0501 decide whether to activate over-temperature protection and battery connect situation according to the voltage value of temperature compare input VT.

Set the value of R18, Li-ion battery charging chip CHK0501 determine whether the Li-ion battery is full according to the voltage value of current detect input CS.

3. How to use intelligent charger?

- (1) After charger and intelligent charger is connected, the charger plug in matching city power grid, the intelligent charger indicator light flash one time and go into the pre-charge state mean that the battery can be charged normally; after insert battery pack the red light flash constantly means it is charging.
- (2) When the green light flash constantly means the battery pack charging has been completed.
- (3) When insert the battery pack and the battery voltage is lower than 6V (can not turn on the radio means less than 6V), the red light flashes, means the battery charger is trickle charging, this procedure will be lasted about 10 minutes; When the red light flash constantly, means charge normally.
- (4) When insert the battery pack and the battery voltage is higher than 6V, the red light flashes, please make sure that batteries and intelligent Charger is connected well.

3. Parts list

| Specification | Usage/function | Package | Bit NO. | Quantity |
|---------------|----------------|---------|---------|----------|
| 0.01uF | Capacitor | C130050 | C62 | 1 |
| CH0501 | IC | SO-8 | U11 | 1 |
| 0R | Resistor | 1206 | R38 | 1 |

| 100K | Resistor | 0805 | R20 R11 | 2 |
|-----------|------------------------|-----------------|---------------------------------|---|
| 100R | Resistor | R-3518 | R45 | 1 |
| 100uF/25V | Electrolytic Capacitor | E-06524S | E12 | 1 |
| 102P | Capacitor | 0805 | C55 | 1 |
| 102P | Capacitor | CP0603 | C13 | 1 |
| 102/400V | Capacitor | PCBCOMPONENT | C52 | 1 |
| 103P | Capacitor | 0805 | C12 C17 | 2 |
| 104P | Capacitor | 0805 | C44 C41 C11 C20 C16 C42 C19 C15 | 8 |
| 105P | Capacitor | 0805 | C32 | 1 |
| 10uF/25V | Electrolytic Capacito | E-05225S | E56 | 1 |
| 10uF/400V | Electrolytic Capacito | E-10245S | E51 | 1 |
| 1K | Resistor | R-3518 | R42 R41 | 2 |
| 1K | Resistor | 805 | R12 | 1 |
| 1N4007 | Diode | DIO3 | D63 D64 D61 D62 | 4 |
| 1N4148 | Diode | DIO3 | D12 D11 | 2 |
| 1R2 | Resistor | 1206 | R22 R21 | 2 |
| 200R | Resistor | 805 | R16 R17 | 2 |
| 220R | Resistor | 1206 | R31 | 1 |
| 220uF/25V | Electrolytic Capacito | E-06524S | E41 | 1 |
| 22K/1% | Resistor | 805 | R39 R15 | 2 |
| 2K/1% | Resistor | 805 | R19 | 1 |
| 330R | Resistor | R-3518 | R46 R43 | 2 |
| 360K | Resistor | 1206 | R51 | 1 |
| 4148 | Diode | 1206 | D15 D14 | 2 |
| 470P | Capacitor | CP0603 | C14 | 1 |
| 470uF/25V | Electrolytic Capacito | E-08235S | E43 | 1 |
| 471/1KV | Capacitor | C-6725 | C51 C45 | 2 |
| 47K/1% | Resistor | 0805 | R35 R34 R36 R37 | 4 |
| 4.7K | Resistor | 0805 | R18 | 1 |
| 5.1V | Diode | 0805 | D18 | 1 |
| 56R | Resistor | R-3518 | R44 | 1 |
| 60UH/1A | Inductor | AXIAL0.15 | L41 | 1 |
| B772 | Triode | T-TO126S-2SB772 | T11 | 1 |
| BATT | Battery contact piece | BATTERY4 | JP11 | 1 |
| CR-2 | | DIP4A | U53 | 1 |
| DS-208 | DC Socket | JK-DS-208 | JK11 | 1 |
| EE13 | Voltage Transformer | TR-1 | TR44 | 1 |
| FR107 | Diode | DIO3 | D51 D57 | 1 |
| FUSE | Fuse | FUSE-1 | F62 | 1 |
| JP2 | AC Socket | JK-2123-2-PP | JP12 | 1 |
| LED-GR | Bicolor lamp | D-0425 | D13 | 1 |
| SR2100 | Diode | D-3435S | D44 | 1 |
| SS14 | Diode | 1812 | D32 | 1 |
| TL431 | Stabilivolt | U-TO92-78LXX | D42 | 1 |
| 1L431 | | 1 | | |
| TR-2 | Conductor | TR1510 | TR62 | 1 |

4. PC board diagram and schematic diagram

